
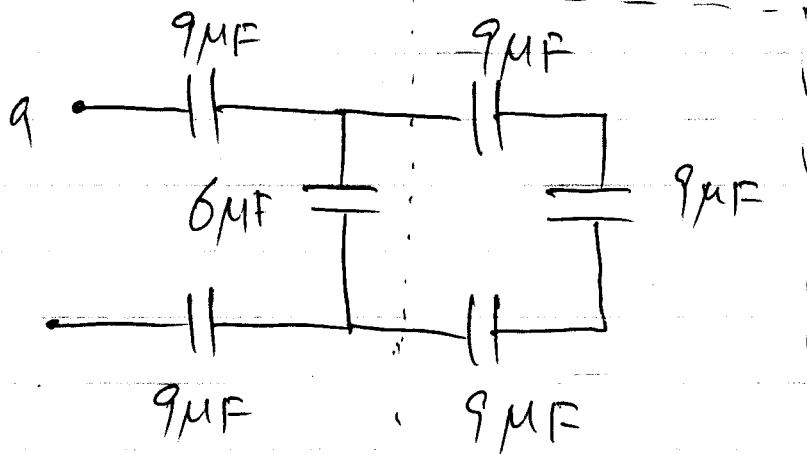


# Solutions to 9C-A MT#2 (W-2008)



1-(a)

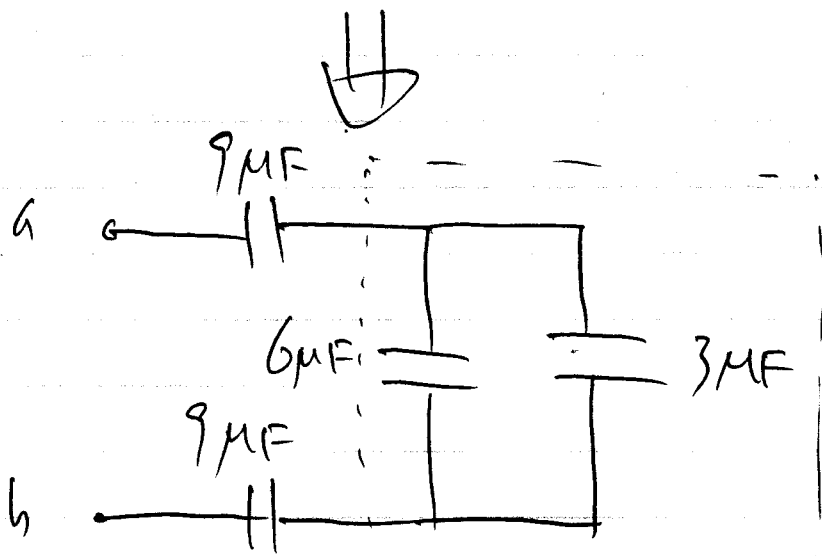


in series




in parallel

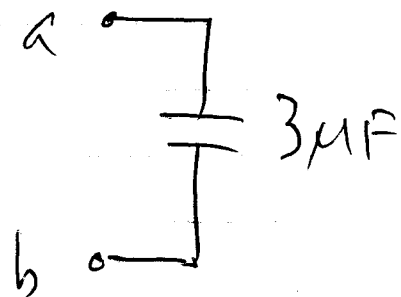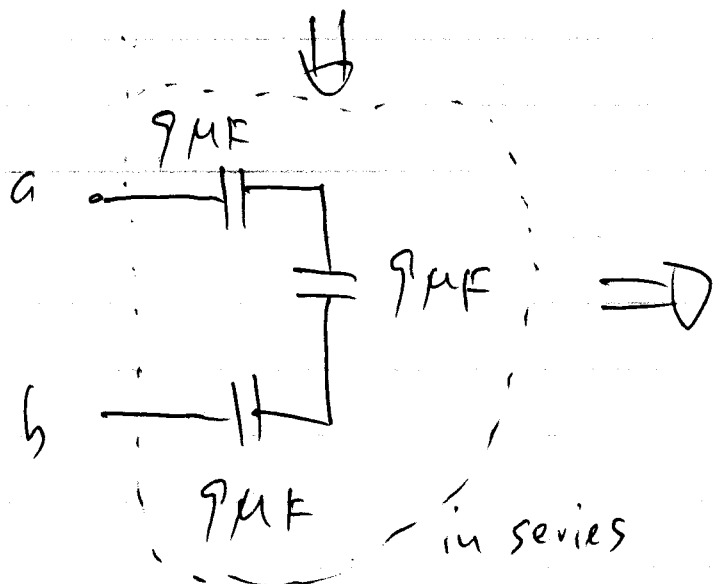

1-(b)

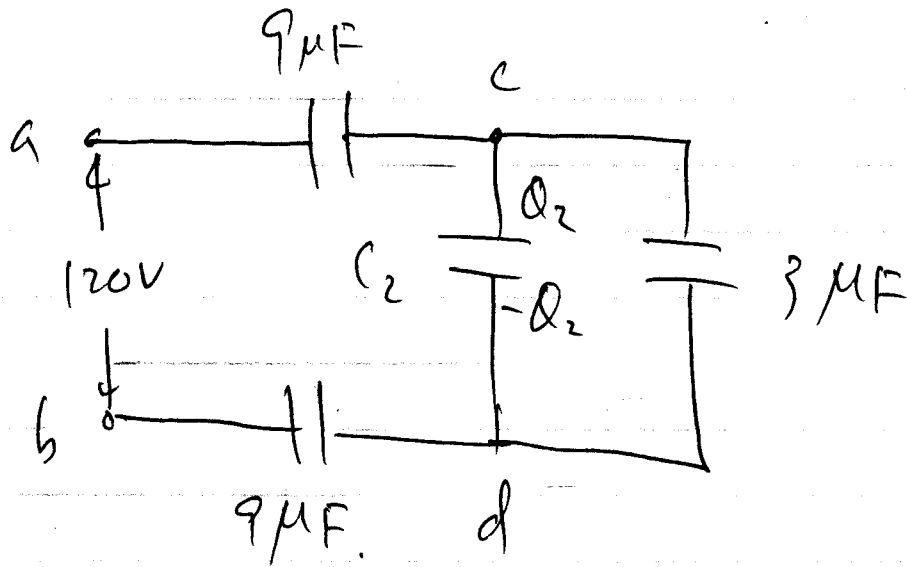

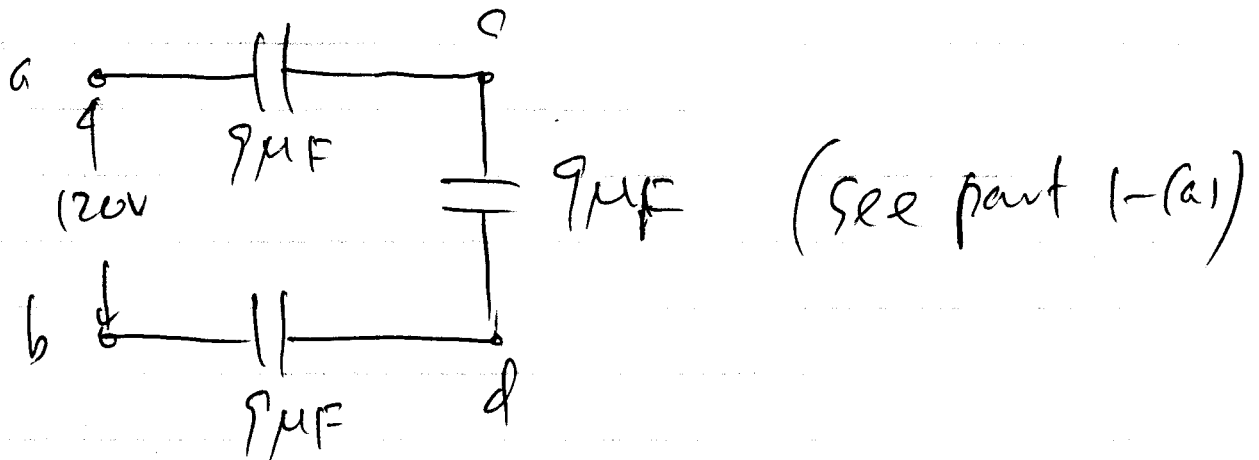To find the charge  $Q_2$  on  $C_2$ , we need to know the potential drop across  $C_2$ , i.e.,  $V_c - V_d \equiv V_{cd}$ . Since




we have  $V_{cd} = \frac{1}{3} (V_{ab}) = 40V$ .

from  $Q_2 = C_2 \cdot V_{cd}$  we have

$$Q_2 = (6 \mu F)(40 \text{ volts}) = 240 \mu C \#$$

2-(a)

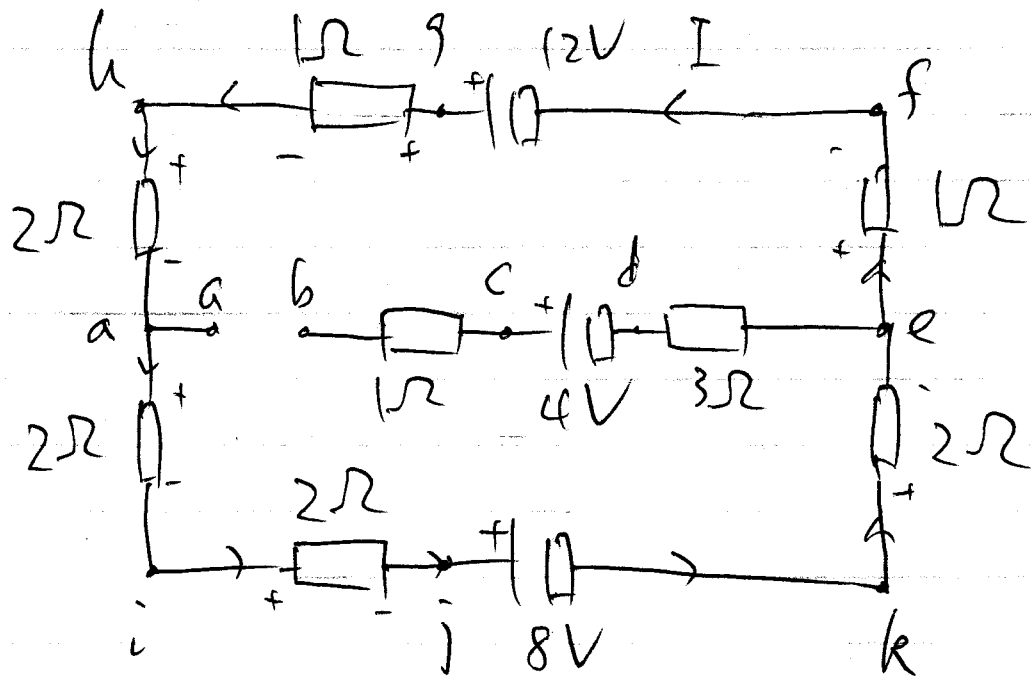

The potential difference between a and b is the difference between  $V_{ae} - V_{be}$ :

$$V_{ab} = V_{ae} - V_{be} = (V_a - V_e) - (V_b - V_e) \dots (1)$$

Since a and b are disconnected, there is no current flowing from b to e, as a result,

$$\begin{aligned} V_{be} &= V_b - V_e = (V_b - V_c) + (V_c - V_d) + (V_d - V_e) \\ &= V_c - V_d = 4 \text{ volts} \dots (2) \end{aligned}$$

So, we only need to find  $V_a - V_e$  to obtain  $V_{ab}$  from (1). To do so, we need to find the current that flows through the outer loop as assigned.

Starting at point a and counter-clockwise along the outer loop, we apply the loop rule:

$$2I + 2I + 8 + 2I + I - 12 + I + 2I = 0$$

$$\therefore 10I = 4 \text{ V} \quad I = \frac{2}{5} \text{ A}$$

Then

$$V_a - V_e = 2I + 2I + 8 + 2I$$

$$= 6I + 8 \text{ volts}$$

$$= 10 \frac{2}{5} \text{ volts}$$

Thus


$$V_{ab} = V_a - V_b = (V_a - V_e) - (V_b - V_e)$$

$$= 10 \frac{2}{5} \text{ volts} - 4 \text{ volts}$$

$$= 6 \frac{2}{5} \text{ volts}$$

2-(9)

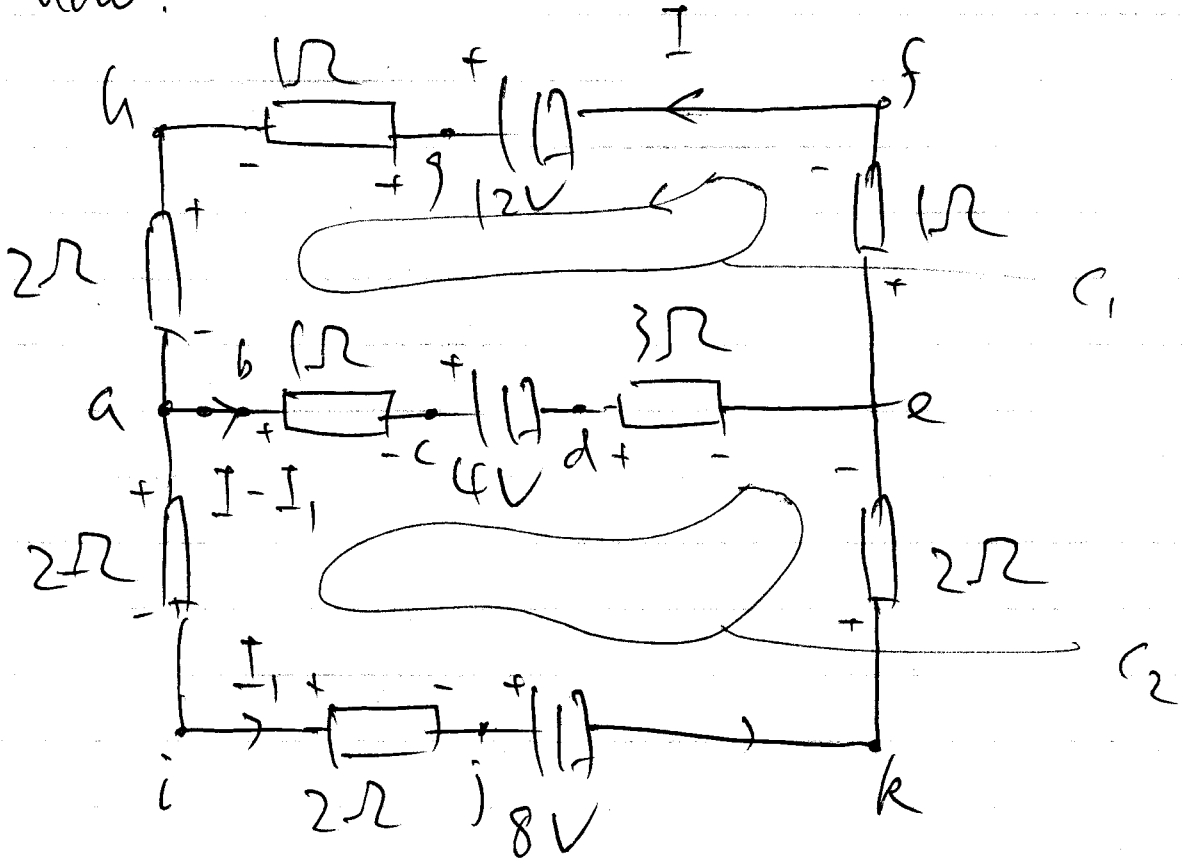When a and b are connected, there will be a current flowing between a and e now.



Assign  $I$  and  $I_1$  as two unknowns, and apply the junction rule at a and e.

Along loop  $C_1$ , and counter-clockwise from a:

$$4(I - I_1) + 4 + 4I - 12 = 0 \quad \dots \textcircled{1}$$

or

$$2I - I_1 = 2 \quad \dots \dots \dots \textcircled{1}'$$

Along Loop  $C_2$  counter-clockwise from a:

$$6I_1 + 8 - 4(I - I_1) - 4 = 0 \dots \textcircled{2}$$

or,


$$2I - 5I_1 = 2 \dots \textcircled{2}$$

Thus  $I_1 = 0$

$$I = 1A$$

The current through the 12-V battery  
is  $I = 1A$

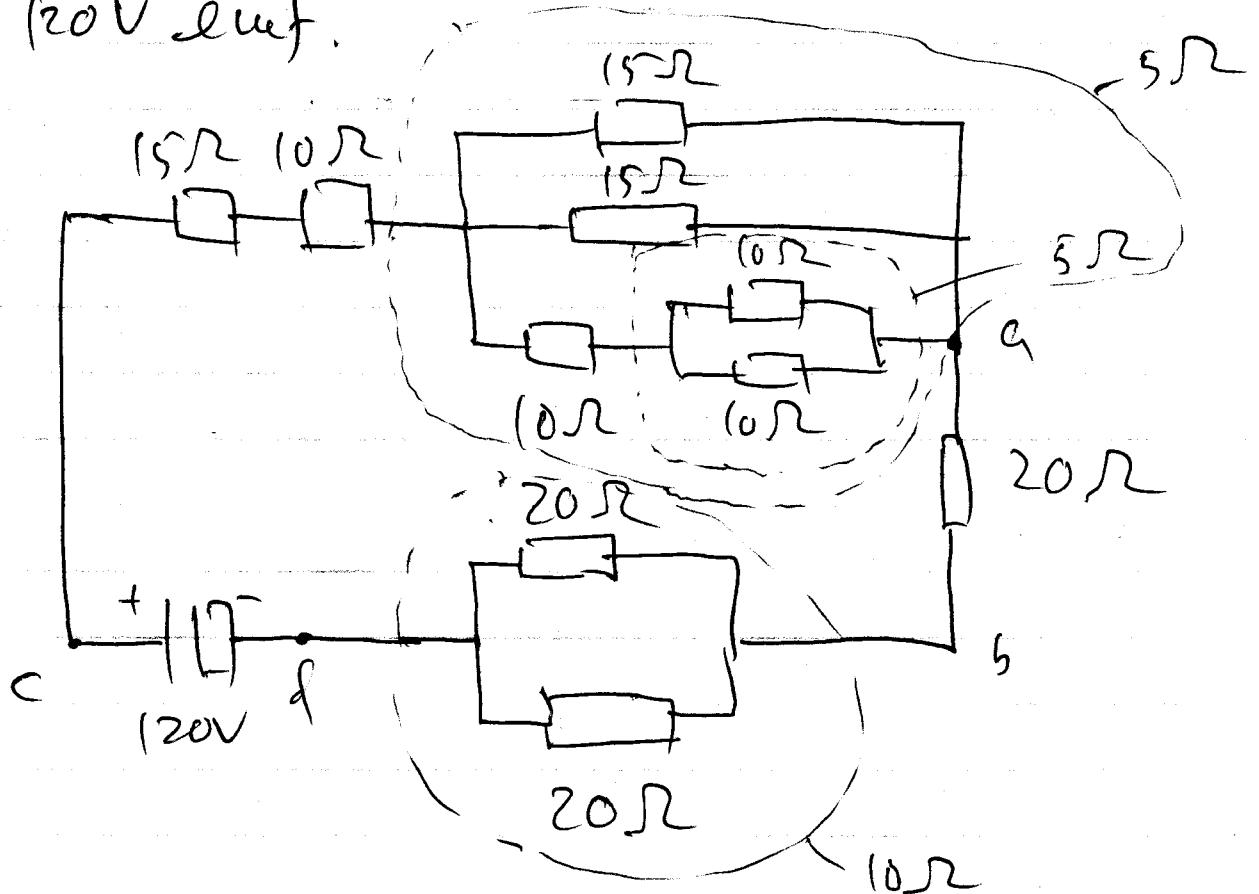3. We need to find the current through the  $20\Omega$  resistor between a and b. To do that we need to determine the equivalent resistance between the two ends of the  $120V$  def.




The total resistance between c and d is

$$R_{cd} = 15 + 10 + 5 + 20 + 10 = \cancel{60} 60\Omega$$

$$\therefore I = \frac{120V}{R_{cd}} = \frac{120V}{60\Omega} = 2A$$

$$\therefore P_{20\Omega} (\text{between a \& b}) = I^2 R = (2A)^2 (20\Omega) = 80 \text{ Watt}$$

4-(a)

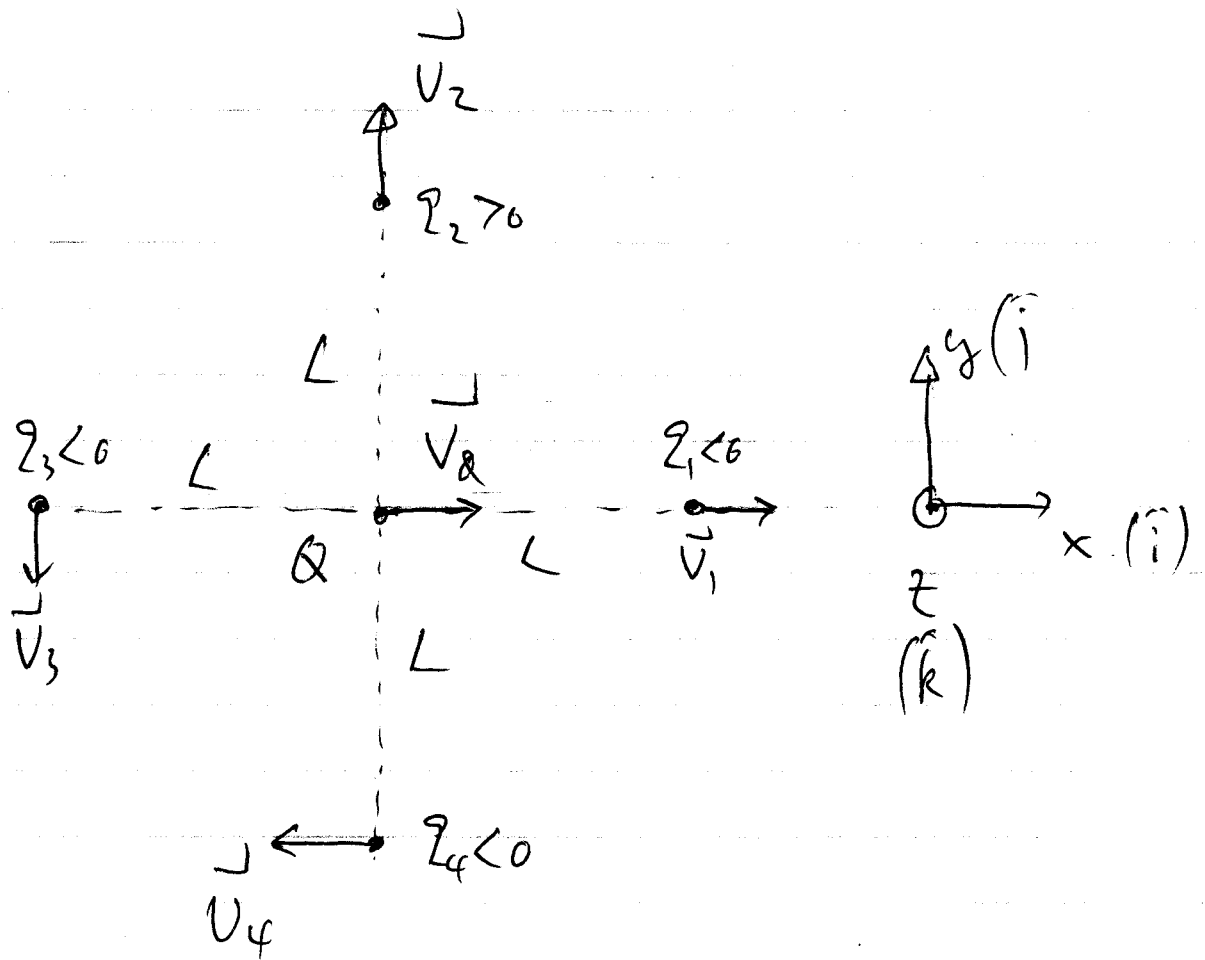

$$\begin{aligned}
 \vec{F} \text{ on } q_1 &= \frac{M_0}{4\pi\epsilon_0} \frac{q_1 q_2}{L^2} \vec{V}_1 \times (\vec{V}_2 \times \hat{i}) \\
 &= \frac{M_0}{4\pi\epsilon_0} \frac{q_1 q_2 V_1 V_2}{L^2} (\hat{i} \times (\hat{j} \times \hat{i})) \\
 &= 0
 \end{aligned}$$

$$\begin{aligned}
 \vec{F} \text{ on } q_2 &= \frac{M_0}{4\pi\epsilon_0} \frac{q_2 q_1}{L^2} V_2 V_1 [\hat{j} \times (\hat{i} \times \hat{j})] \\
 &= - \frac{M_0}{4\pi\epsilon_0} \frac{q_2 q_1}{L^2} V_2 V_1 \hat{i}
 \end{aligned}$$



$$\vec{F}_{Q \text{ on } Q_3}^{(M)} = \frac{M_0}{4\pi} \frac{Q_3 Q V_3 V_Q}{L^2} \left[ (-\hat{j}) \times (\hat{i} \times (-\hat{i})) \right]$$

$$= 0$$


$$\vec{F}_{Q \text{ on } Q_4}^{(M)} = \frac{M_0}{4\pi} \cdot \frac{Q_4 Q \cdot V_4 V_Q}{L^2} \left[ (-\hat{i}) \times (\hat{i} \times (-\hat{j})) \right]$$

$$= \frac{M_0}{4\pi} \cdot \frac{Q_4 Q \cdot V_4 V_Q}{L^2} \left( (-\hat{i}) \times (-\hat{k}) \right)$$


$$= -\frac{M_0}{4\pi} \cdot \frac{Q_4 Q \cdot V_4 V_Q}{L^2} \hat{j}$$

4-(b)
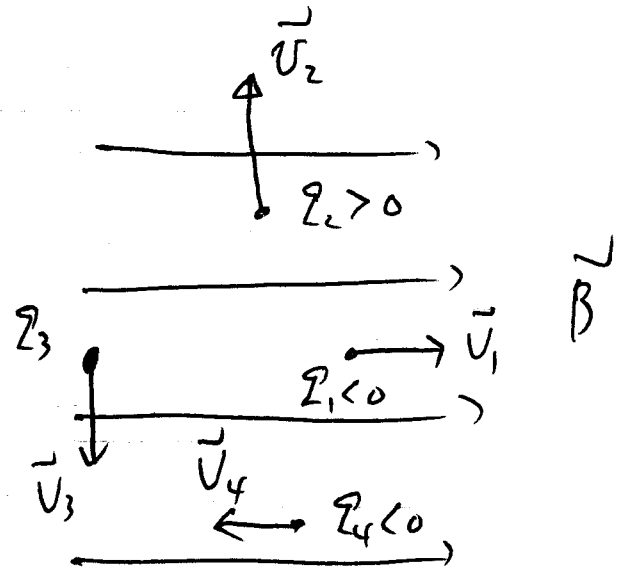
$$\begin{aligned} \vec{F}_{\text{on } q_1}^{(M)} &= q_1 \vec{v}_1 \times \vec{B} \\ &= q_1 v_1 B (\hat{i} \times \hat{i}) \\ &= 0 \end{aligned}$$


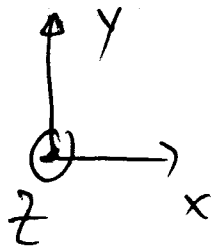
$$\begin{aligned} \vec{F}_{\text{on } q_2}^{(M)} &= q_2 \vec{v}_2 \times \vec{B} \\ &= q_2 v_2 B (\hat{j} \times \hat{i}) \\ &= -q_2 v_2 B \hat{k} \end{aligned}$$



$$\begin{aligned} \vec{F}_{\text{on } q_3}^{(M)} &= q_3 \vec{v}_3 \times \vec{B} \\ &= q_3 v_3 B (-\hat{j} \times \hat{i}) \\ &= q_3 v_3 B \hat{k} \end{aligned}$$

$$\begin{aligned} \vec{F}_{\text{on } q_4}^{(M)} &= q_4 \vec{v}_4 \times \vec{B} \\ &= q_4 v_4 B (-\hat{i} \times \hat{i}) \\ &= 0 \end{aligned}$$

5-(a)

$$\vec{F}_{\text{on the wire}} = \vec{F}_{\text{on } ab} + \vec{F}_{\text{on } bc} + \vec{F}_{\text{on } cd} \\ + \vec{F}_{\text{on } de} + \vec{F}_{\text{on } ef}$$

$$\vec{F}_{\text{on } ab} = I \vec{ab} \times \vec{B} = 0$$

$$\vec{F}_{\text{on } bc} = I \vec{cb} \times \vec{B} \\ = (6A)(0.5T)(0.5m) (-\hat{i} + \hat{j}) \times \hat{i} \\ = -1.5N \hat{k}$$

$$\vec{F}_{\text{on } cd} = I \vec{cd} \times \vec{B} \\ = (6A)(0.5T)(0.5m) (-\hat{k} \times \hat{j}) \\ = -1.5N \hat{j}$$

$$\vec{F}_{\text{on } de} = I \vec{de} \times \vec{B} = (6A)(0.5T)(0.5m) (\hat{i} + \hat{j}) \times \hat{i} \\ = 1.5N \hat{k}$$

$$\vec{F}_{\text{on } ef} = I \vec{ef} \times \vec{B} = (6A)(0.5T)(0.5m) (-\hat{i}) \times (\hat{i}) = 0$$

Thus the net force on the wire is

$$\vec{F}_{\text{on the wire}} = -1.5\text{N}\hat{j}$$

5-(g)

$$\vec{F}_{\text{on af}} = I \vec{a\hat{f}} \times \vec{B}$$

$$= (0.5\text{T})(0.5\text{m})(6\text{A})(\hat{k} \times \hat{i})$$

$$= +1.5\text{N}\hat{j}$$

$$\vec{F}_{\text{on af}} = -\vec{F}_{\text{on abcdef}}$$

\*