

Solutions to PL-C Midterm #2 (2021)

$$1-(a) \quad C_{12} = C_1 + C_2 = 15 \mu\text{F}$$

$$C_{45} = C_4 + C_5 = 30 \mu\text{F}$$

$$\begin{aligned} \frac{1}{C_{\text{network}}} &= \frac{1}{C_{12345}} = \frac{1}{C_{12}} + \frac{1}{C_3} + \frac{1}{C_{45}} \\ &= \frac{1}{15} + \frac{1}{15} + \frac{1}{30} = \frac{1}{6} \end{aligned}$$

$$\therefore C_{12345} = 6 \mu\text{F}$$

1-(b) The charge on the network capacitor C_{12345} , Q_{net} , is the same as on C_{12} , C_3 , and C_{45} .

$$Q_{\text{net}} = Q_{45} = V_{45} * C_{1234} = 60 \mu\text{C}$$

\therefore The potential drop across C_4 & C_5 is

$$V_{45} = \frac{Q_{45}}{C_{45}} = \frac{60 \mu\text{C}}{30 \mu\text{F}} = 2\text{V}$$

1-(c) The potential drop across C_1 is the same as the potential drop across C_2 :

$$V_{12} = \frac{Q_{12}}{C_{12}} = \frac{Q_{\text{ext}}}{C_{12}} = \frac{60 \mu\text{C}}{15 \mu\text{F}} = 4\text{V}$$

$$U_{\text{stored}}(C_1) = \frac{C_1}{2} V_{12}^2$$

$$= \frac{1}{2} \times 10 \mu\text{F} \times (4\text{V})^2$$

$$= 80 \mu\text{J}$$


1-(d) The charge stored on C_2 is the potential drop across $V_2 = V_{12}$ times C_2 :

$$Q_2 = V_2 \cdot C_2 = 4\text{V} \times 5 \mu\text{F} = 20 \mu\text{C}$$

2-(a) The two parallel legs have serial resistances of 6Ω ($3\Omega + 3\Omega$) and 12Ω ($5\Omega + 7\Omega$). Thus

$$R_{ef} = \frac{6\Omega \cdot 12\Omega}{6\Omega + 12\Omega} = 4\Omega$$

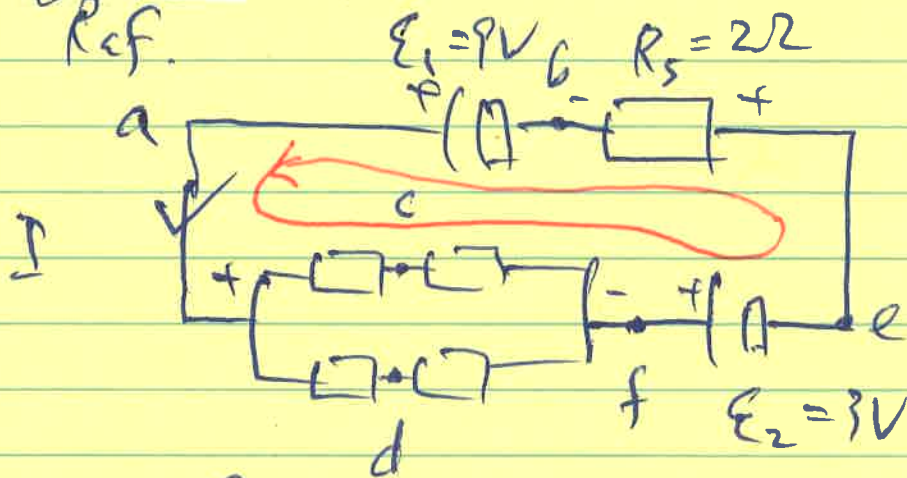2-(b) We need to know the current through R_{ef} .



Let the current be I , counterclockwise, from a counter-clockwise loop:

$$\oint_{a \rightarrow c \rightarrow e \rightarrow f \rightarrow d \rightarrow a} \vec{E} \cdot d\vec{l} = 0 = I \cdot R_{ef} + (+9V) + I \cdot R_5 + (-3V)$$

$$\therefore I = \frac{9V - 3V}{R_{ef} + R_5} = \frac{6V}{6\Omega} = 1A$$

$$\therefore V_{af} = V_a - V_f = I \cdot R_{ef} = 4V$$

2-c) The current through 7Ω resistor is the potential drop V_{ef} divided by the resistance of the $5\Omega + 7\Omega$ leg:


$$I(7\Omega) = \frac{V_{ef}}{5\Omega + 7\Omega} = \frac{4V}{12\Omega} = \frac{1}{3} A$$

$$P(7\Omega) = I^2(7\Omega) * 7\Omega = \left(\frac{1}{3} A\right)^2 * 7\Omega$$

$$= \frac{7}{9} \text{ Watt.}$$

✖

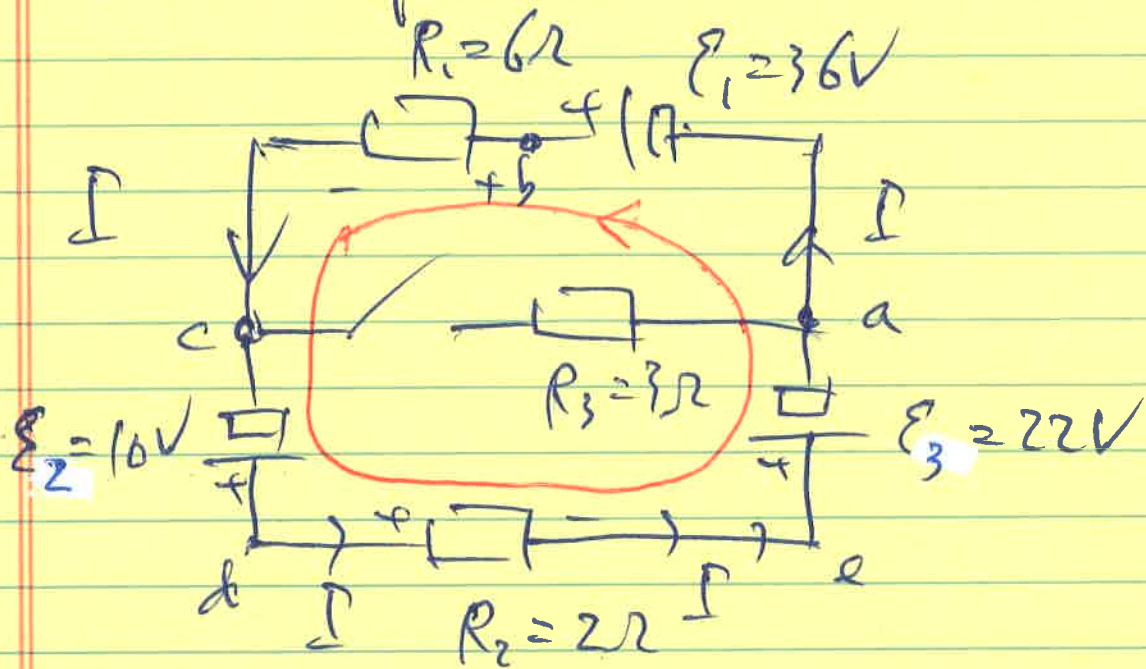3-(a) The only current is the one along the outer loop:



Let the current be I as assigned.


$$\oint \vec{E} \cdot d\vec{l} = 0 = -36 + 6I - 10 + 2I + 22$$

abcdea

$$\therefore I = \frac{36 + 10 - 22}{6 + 2} = 3A$$

There is no current through $R_3 = 3\Omega$.
The currents through R_1 and R_2 are the same, $I = 3A$.

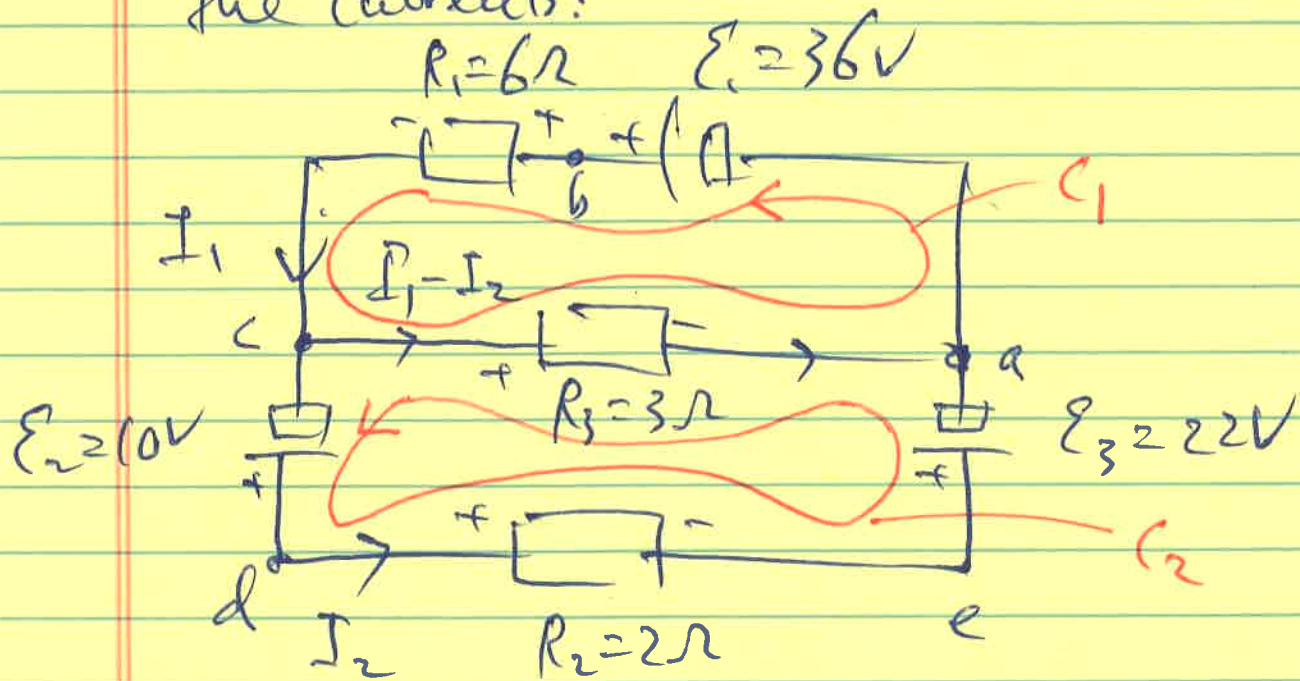3-(b) When S is closed, we have two loops and need Kirchoff's rules to solve for the currents:



Along Loop¹:

$$\oint_{abca} \vec{E} \cdot d\vec{l} = -36 + 6I_1 + 3(I_1 - I_2) = 0$$

$$\therefore 9I_1 - 3I_2 = 36$$

$$\Rightarrow \boxed{3I_1 - I_2 = 12} \quad \text{--- (1)}$$

Along Loop²:

$$\oint_{acdea} \vec{E} \cdot d\vec{l} = -3(I_1 - I_2) - 10 + 2I_2 + 22 = 0$$

$$\Rightarrow \boxed{3I_1 - 5I_2 = 12} \quad \text{--- (2)}$$

① - ② :

$$4I_2 = 0 \quad \therefore I_2 = 0$$

From ① and $I_2 = 0$,

$$I_1 = 4A$$

Thus the currents through R_1 and R_3 are 3A; while there is no current flowing through R_2 *

$$\begin{aligned} 3-(c) \quad V_{bd} &= V_b - V_d = (V_b - V_c) + (V_c - V_d) \\ &= 6I_1 + (-10V) = 14V \end{aligned}$$


Or

$$\begin{aligned} V_{bd} &= (V_b - V_a) + (V_a - V_c) + (V_c - V_d) \\ &= 36V - 12V - 10V = 14V \end{aligned}$$

Or

$$\begin{aligned} V_{bd} &= (V_b - V_c) + (V_c - V_e) + (V_e - V_d) \\ &= 36V + 0 \times (2\Omega) - 22V = 14V \end{aligned}$$

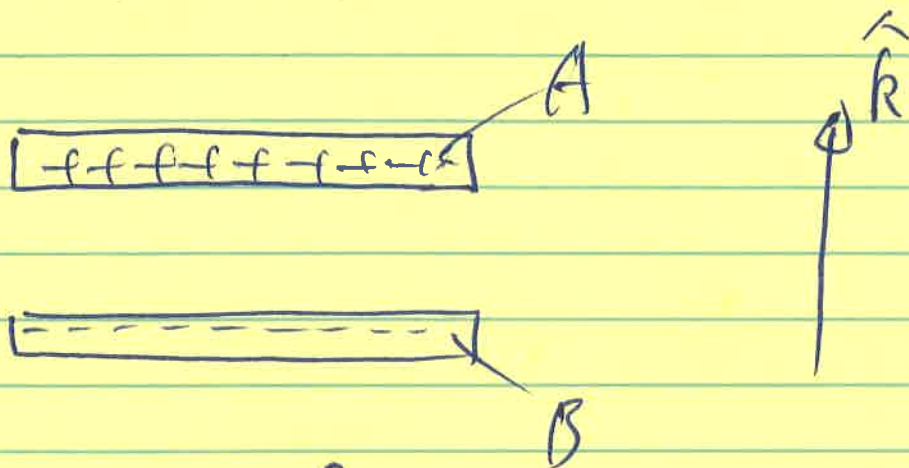4-(a) The electric field produced by charges on Plate B at Plate A is



$$\vec{E}_B(\text{at } A) = \frac{Q_B}{2\epsilon_0 S} \cdot \hat{k} = \frac{Q}{2\epsilon_0 S} (-\hat{k})$$

So the force exerted on charge Q on Plate A is

$$\vec{F}_{on A} = Q \cdot \vec{E}_B(\text{at } A) = \frac{Q^2}{2\epsilon_0 S} (-\hat{k})$$

4-(b) The work done by the external force when plate A is moved up by $d = d \hat{k}$ is

$$\begin{aligned} W_{ext} &= \vec{d} \cdot \vec{F}_{ext} = \vec{d} \cdot (-\vec{F}_{on A}) \\ &= \frac{1}{2} \frac{Q^2}{\epsilon_0 S} d \end{aligned}$$

$$4-c) \quad W_{\text{ext}} = \frac{1}{2} \frac{d}{\epsilon_0 s} Q^2 = \frac{Q^2}{2(\epsilon_0 s/d)} = \frac{Q^2}{2C}$$